



Common cathode 7-segment display and 7448 common cathode driver

The 7448 chip provides high output signals to light the segments but they cannot source much current. Therefore, place external pull-up resistors from the cathodes on the display to V_{cc} . These resistors limit current to the LED's when on and to the 7448 when off.